



EXPERIMENT – 06

NAME – SURAJ
ROLL NO. -2201769

EEM614 (VLSI Lab)

(a) To realize CMOS inverter using CD4007 IC and perform the transient analysis with and without load at different input frequencies.

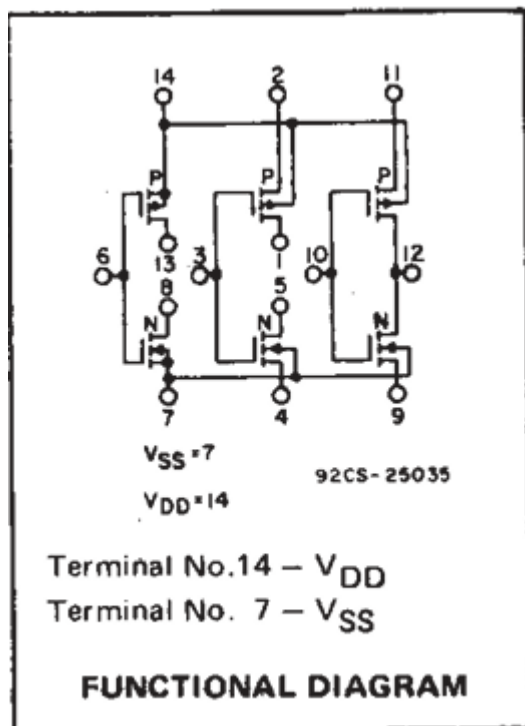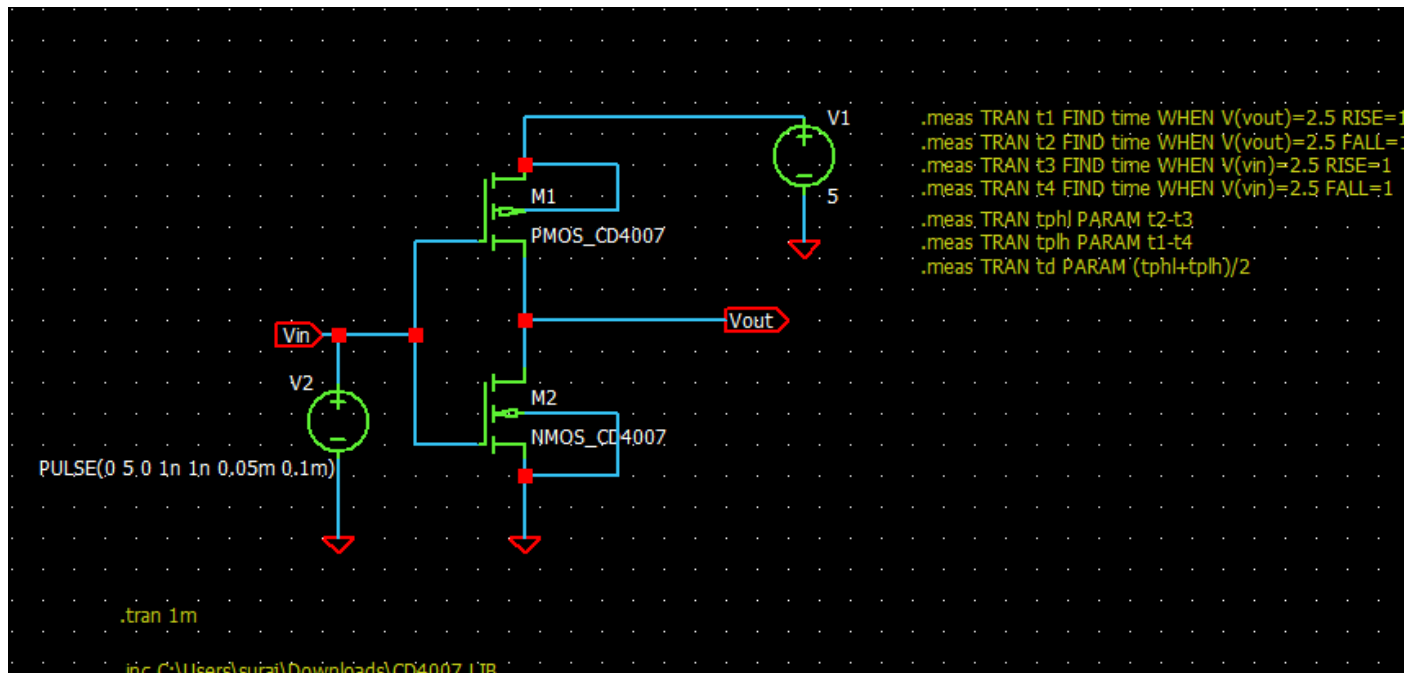
(b) To realize 3-stage CMOS ring oscillator using CD4007 IC and calculate the oscillation frequency.




Drain 2Dp	1	14	VDD
Source 2Sp	2	13	Drain 1Dp
Input 2A	3	12	Output 3Y
Source 2Sn	4	11	Source 3Sp
Drain 2Dn	5	10	Input 3A
Input 1A	6	9	Source 3Sn
VSS	7	8	Drain 1Dn

1. WITHOUT LOAD


At 10 KHz

 


At 100 KHz

 


At 600 KHz

 


At 1000 KHz

 

At 3000 KHz

 


At 5000 KHz

 


2. WITH LOAD 30PF


At 10 KHz

 


At 100 KHz

 


At 600 KHz

 


At 1000 KHz

 

At 3000 KHz

 

At 5000 KHz

 

Simulation Results:

1.WITHOUT LOAD

WITHOUT LOAD				
Sr.no.	Frequency(kHz)	Rise Time	Fall time	Delay
1.	5	5.78284e-10	5.21393e-10	5.49838e-10
3.	50	5.75303e-10	5.21393e-10	5.48348e-10
4.	100	5.75022e-10	5.21393e-10	5.48207e-10
5.	200	5.75303e-10	5.2025e-10	5.47776e-10
6.	400	5.75303e-10	5.2025e-10	5.47776e-10
7.	600	5.75303e-10	5.2025e-10	5.47776e-10
8.	800	5.75303e-10	5.2025e-10	5.47776e-10
9.	1000	5.75303e-10	5.2025e-10	5.47776e-10
10.	1200	5.76496e-10	5.2025e-10	5.48373e-10
11.	1600	5.75303e-10	5.2025e-10	5.47776e-10
12.	2000	5.76496e-10	5.2025e-10	5.48373e-10
13.	3000	5.75303e-10	5.2025e-10	5.47776e-10
14.	4000	5.76271e-10	5.2025e-10	5.48261e-10
15.	5000	5.75615e-10	5.75615e-10	5.47932e-10

2. WITH LOAD 30pF

WITH LOAD 30pF				
Sr.no.	Frequency(kHz)	Rise Time	Fall time	Delay
1.	5	2.49051e-08	2.14262e-08	2.31656e-08
2.	50	2.49051e-08	2.14262e-08	2.31656e-08
4.	100	2.49051e-08	2.14262e-08	2.31656e-08
5.	200	2.49051e-08	2.14262e-08	2.31656e-08
6.	400	2.49051e-08	2.14262e-08	2.31656e-08
7.	600	2.49051e-08	2.14262e-08	2.31656e-08
8.	800	2.49051e-08	2.14262e-08	2.31656e-08
9.	1000	2.49051e-08	2.14262e-08	2.31656e-08
10.	1200	2.49051e-08	2.14262e-08	2.31656e-08
11.	1600	2.49051e-08	2.14262e-08	2.31656e-08
12.	2000	2.49051e-08	2.14262e-08	2.31656e-08
13.	3000	2.42934e-08	2.08256e-08	2.25595e-08
14.	4000	2.42926e-08	2.08256e-08	2.25591e-08
15.	5000	2.42804e-08	2.08256e-08	2.2553e-08

Experimental Results

1.



WITHOUT LOAD				
Sr.no.	Frequency KHz	Rise Time(us)	Fall time(us)	Delay(us)
1.	5	0.0985	0.0227	0.0606
2.	10	0.0985	0.0227	0.0606
3.	30	0.0985	0.0227	0.0606
4.	50	0.0985	0.0227	0.0606
5.	80	0.0985	0.0227	0.0606
6.	100	0.0985	0.0228	0.06065
7.	150	0.0985	0.0227	0.0606
8.	200	0.0985	0.0227	0.0606
9.	300	0.0973	0.0227	0.0606
10.	400	0.0972	0.0227	0.05995
11.	500	0.0972	0.0227	0.05995
12.	800	0.09655	0.0227	0.059625
13.	1000	0.09655	0.0224	0.059475
14.	1500	0.09655	0.0224	0.059475
15.	2000	0.09655	0.0225	0.059525
16.	4000	0.09544	0.022	0.05872
17.	5000	0.09544	0.022	0.05872

2.



WITH LOAD 30pF				
Sr.no	Frequency KHz	Rise Time(us)	Fall time(us)	Delay(us)
1.	5	0.132	0.0311	0.08155
2.	50	0.132	0.0311	0.08155
3.	80	0.132	0.0311	0.08155
5.	100	0.132	0.0311	0.08155
6.	200	0.131	0.0311	0.08105
7.	300	0.13	0.0311	0.08055
8.	400	0.13	0.0311	0.08055
9.	500	0.13	0.0311	0.08055
11.	1000	0.13	0.0311	0.08055
12.	1500	0.13	0.0311	0.08055
13.	2000	0.13	0.0311	0.08055
14.	4000	0.13	0.0311	0.08055
15.	5000	0.13	0.0311	0.08055

SIMULATION VS EXPERIMENTAL

1.WITHOUT LOAD


 
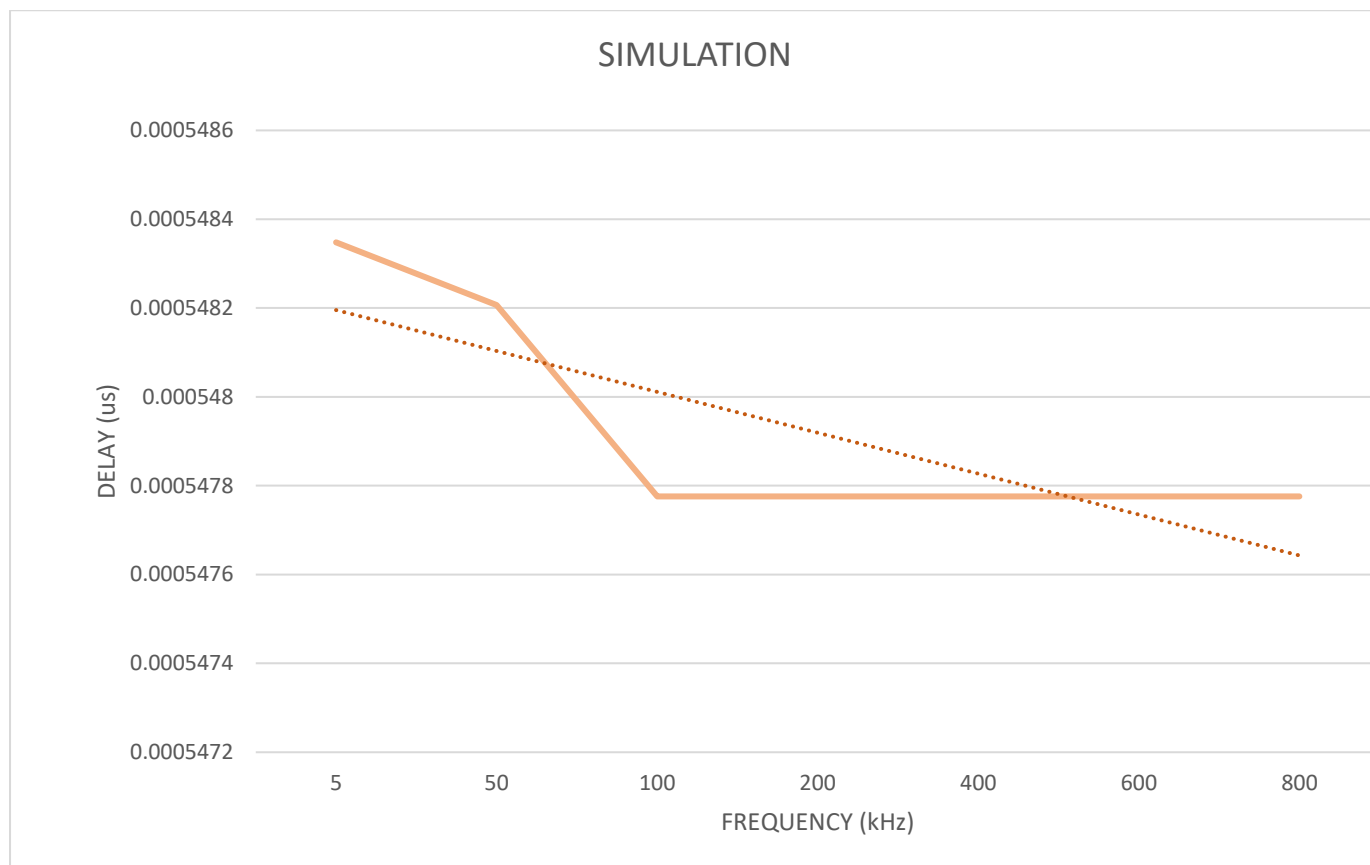


2.WITH LOAD

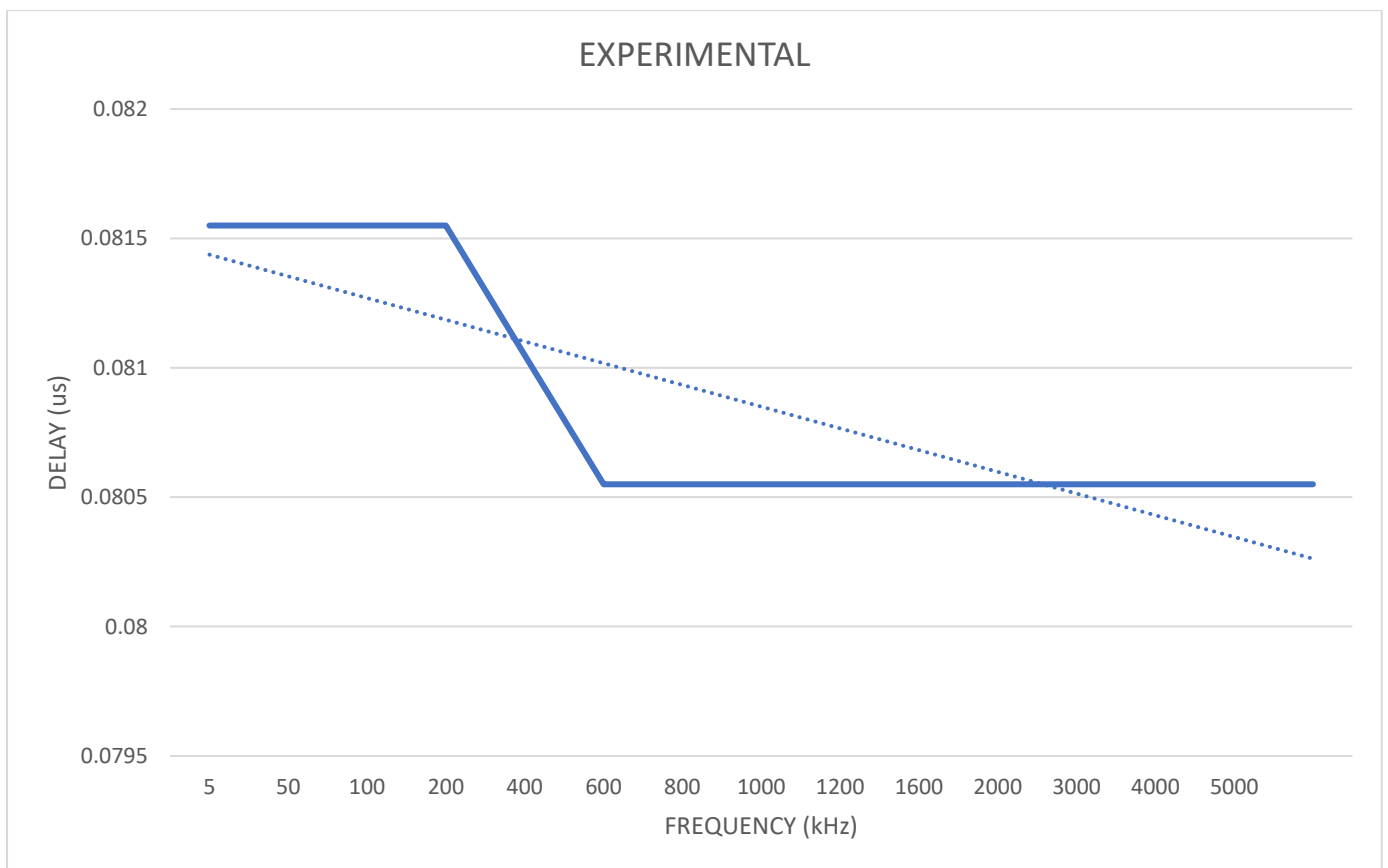
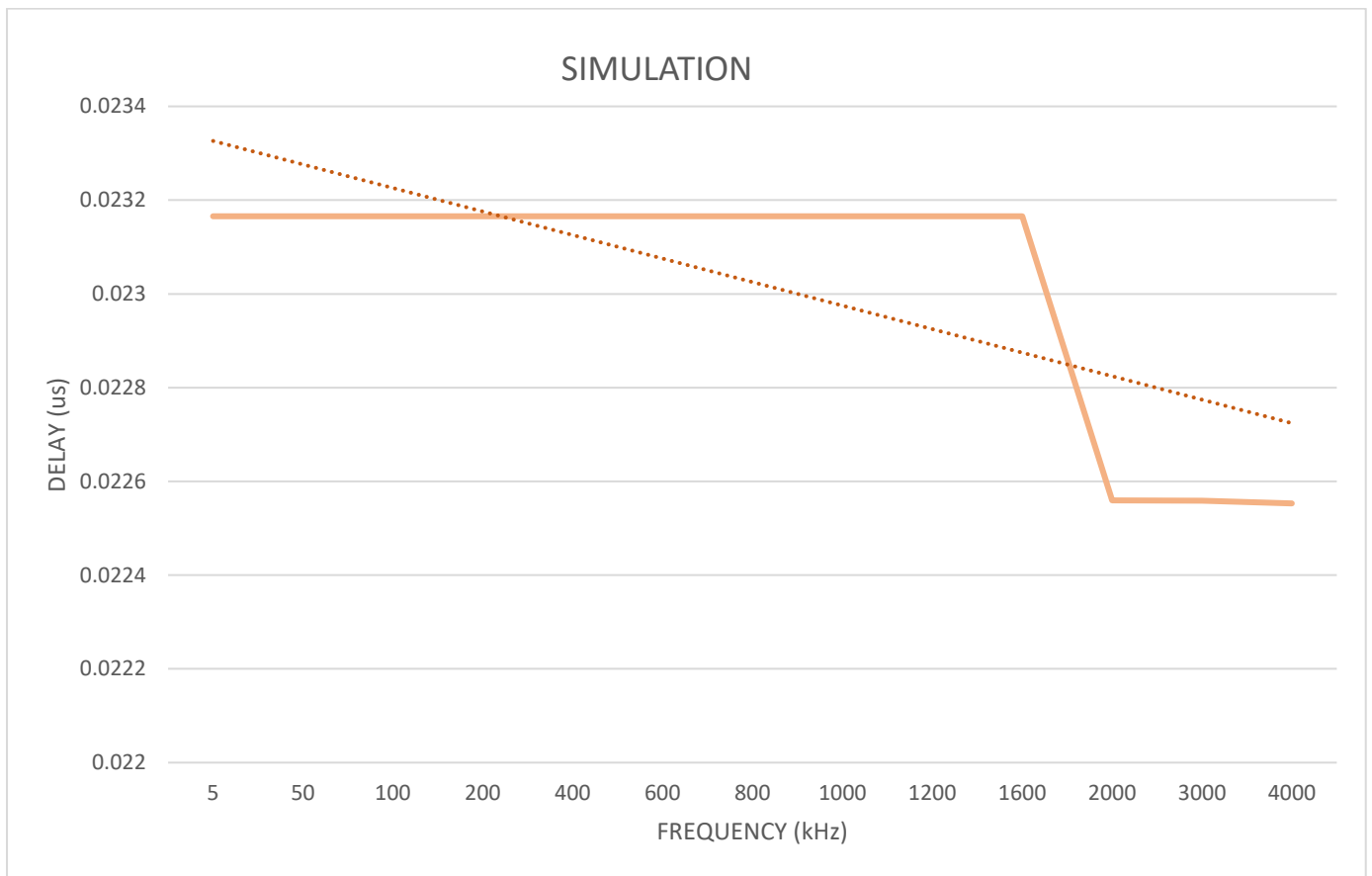





CONCLUSION:

   1. **Impact of Load on Output:** After connecting a load, the inverter output becomes distorted even at low frequencies, indicating that the CD4007 IC struggles with higher loads.
2. **Current-Driving Limitations:** The distortion is caused by the limited current-driving capability of the CD4007 IC, making it unsuitable for high-load applications.
3. **Capacitive Load Effects:** A capacitive load exceeding 50pF results in increased propagation delay and degraded signal integrity, further impacting the inverter's performance.
4. **Recommended Usage:** The CD4007 IC is best suited for low-load, low-frequency applications due to its limitations when driving higher loads.




6(b) 3 STAGE RING OSCILLATOR

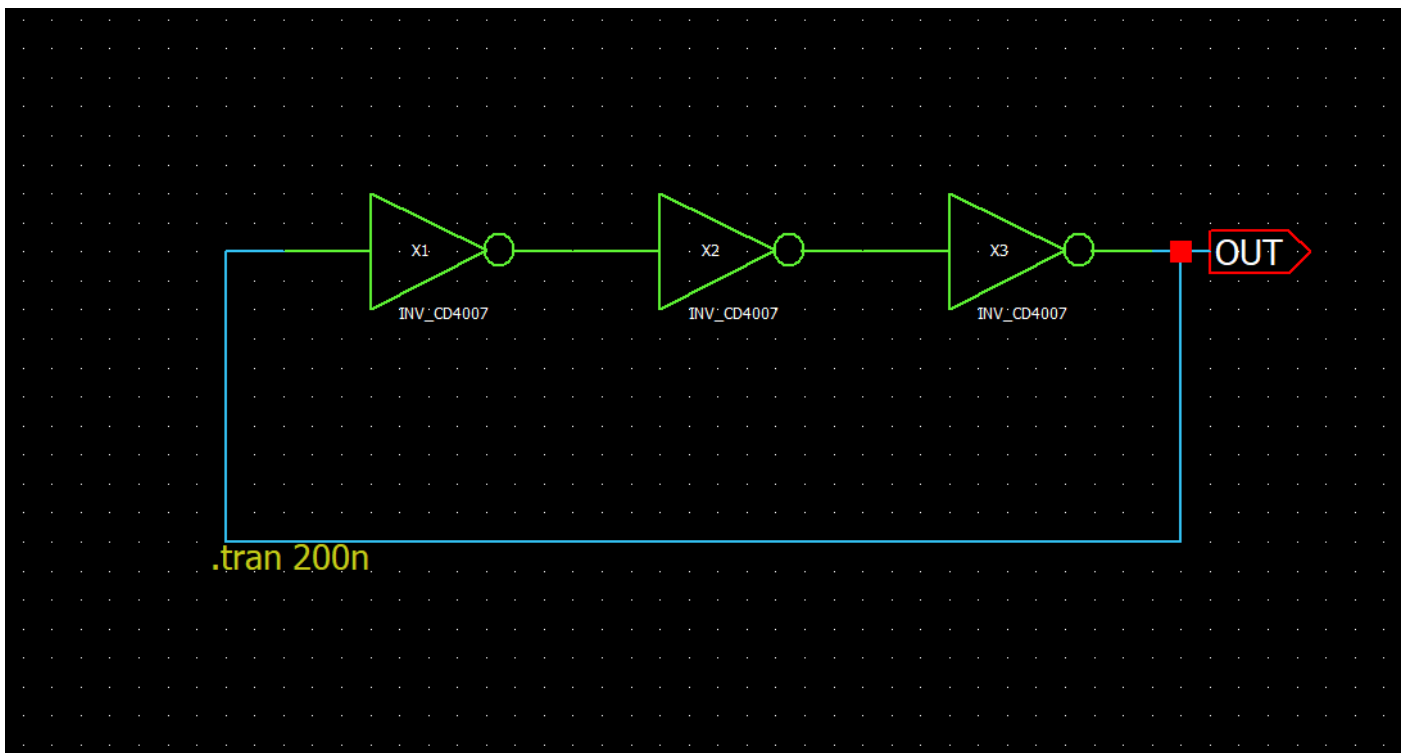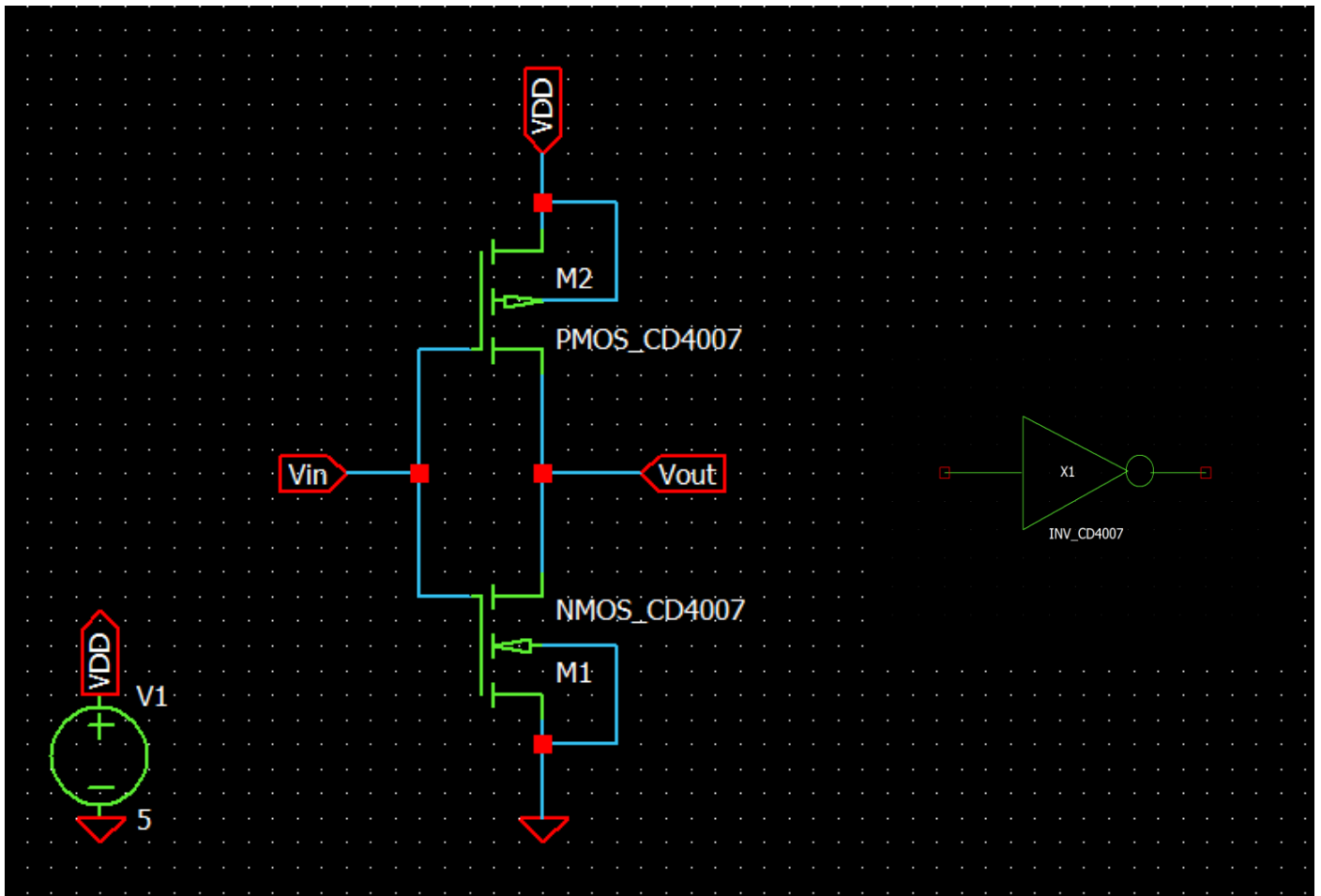

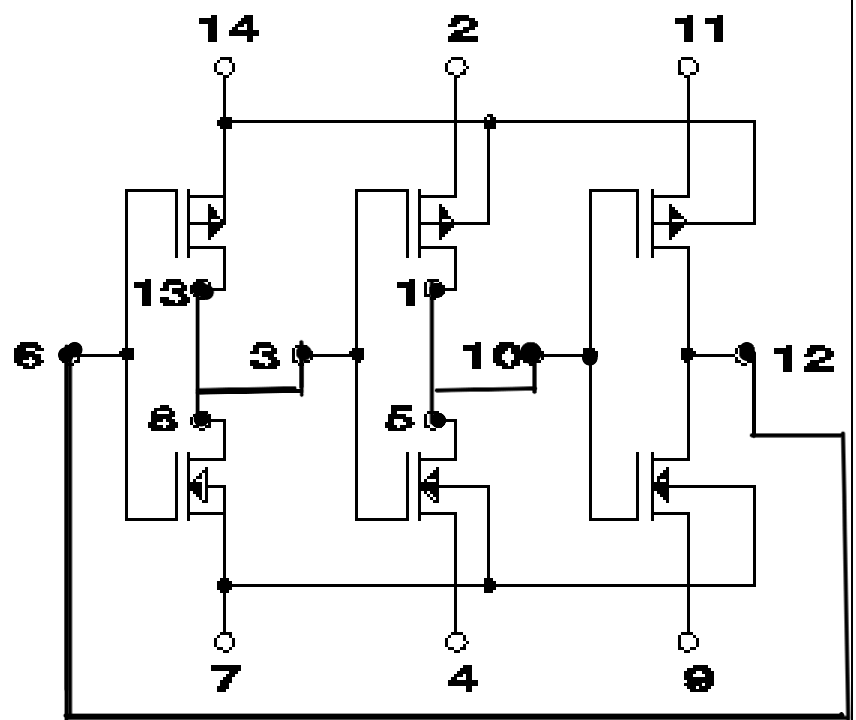 
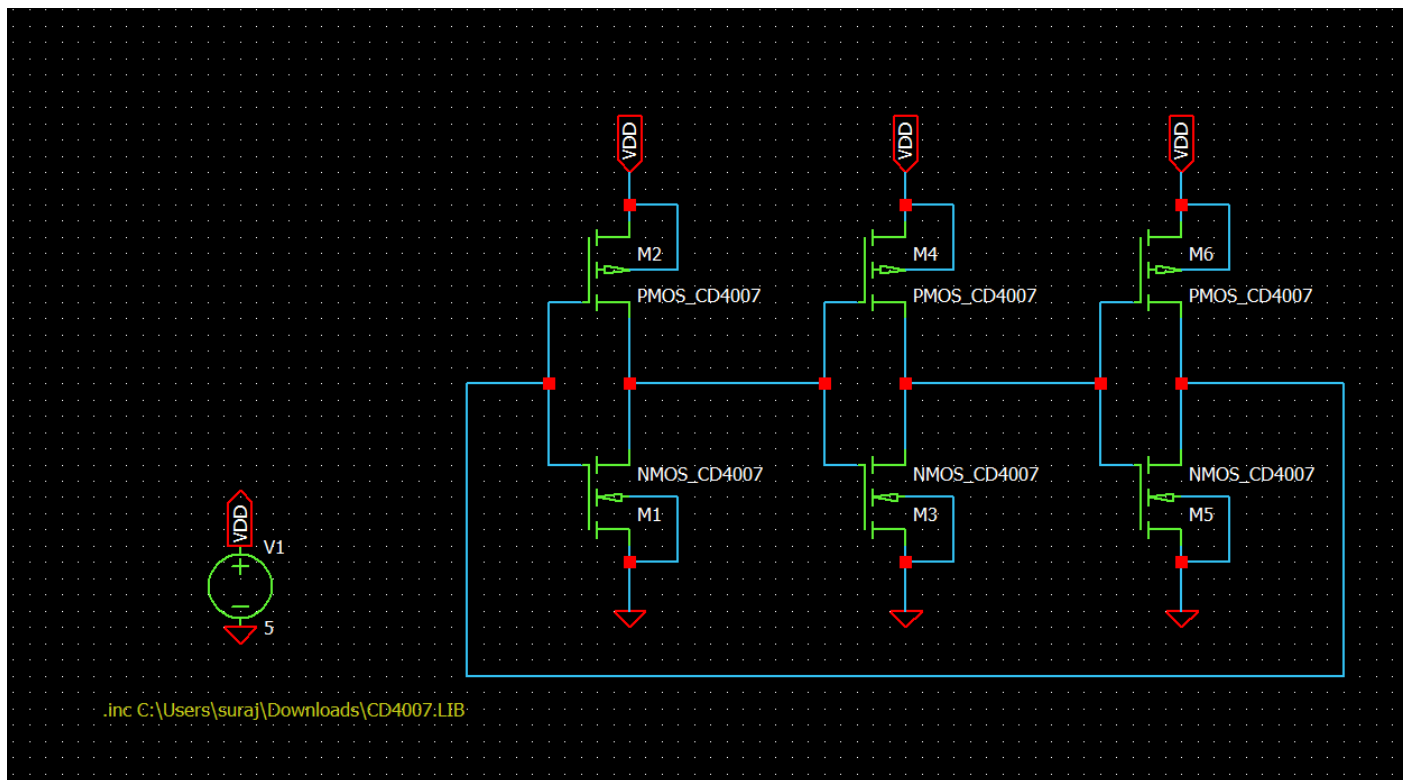


(a) The Connection Diagram

(b) The Schematic Diagram

 

Frequency of Oscillation

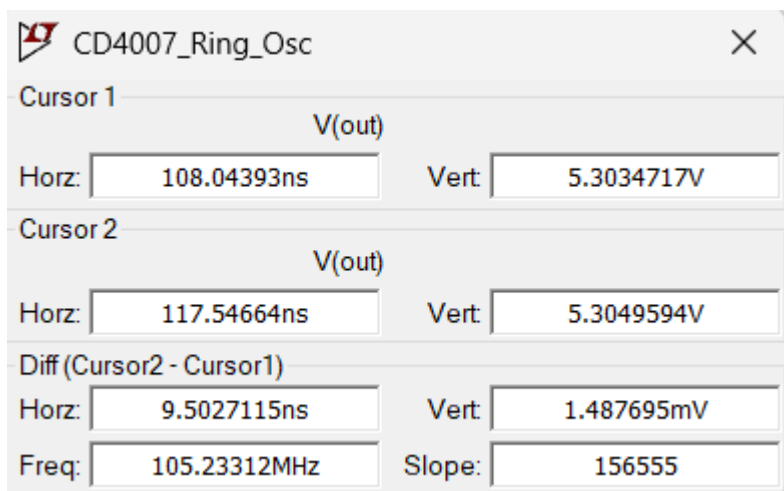 

$$f_{\text{osc}} = 105\text{MHz}$$

Conclusions from the Ring Oscillator Experiment:

1. Oscillation Frequency Discrepancy:

- This large difference highlights the impact of non-idealities in real hardware, such as parasitic capacitances, resistances, and device mismatches.

2. Influence of Parasitic Elements:

- Parasitic capacitances from the breadboard, wiring, and measurement instruments increased the overall delay per stage, significantly reducing the oscillation frequency in the experiment compared to the simulation.

3. Measurement Load Effect:

- The oscilloscope probe introduced additional capacitance, further loading the circuit and reducing the observed frequency during the experiment.

4. Experimental Results can be Improved by following ways:

- Use a PCB instead of a breadboard to reduce parasitic elements.
- Employ proper decoupling capacitors and a stable power supply.
- Include parasitic elements in the simulation for more realistic results.
- Use low-capacitance measurement probes to minimize loading effects.

